

1. An industrial machine has sensors placed at 4 different locations. If one of the following conditions arises the machine has to be stopped and should fire an alarm.

- If sensor 1 and 2 are activated
- If sensor 1 and 4 are activated
- If sensor 2, 3, and 4 are activated

Draw a truth table for the above machine and derive a boolean expression.

2. What is the result of adding the following two numbers?

$$0 + 0 = \dots$$

$$0 + 1 = \dots$$


$$1 + 0 = \dots$$

$$1 + 1 = \dots \text{ and to } \dots$$


3. Fill the following table

| A | B | SUM | CARY |
|---|---|-----|------|
| 0 | 0 | ... | ... |
| 1 | 0 | ... | ... |
| 0 | 1 | ... | ... |
| 1 | 1 | ... | ... |

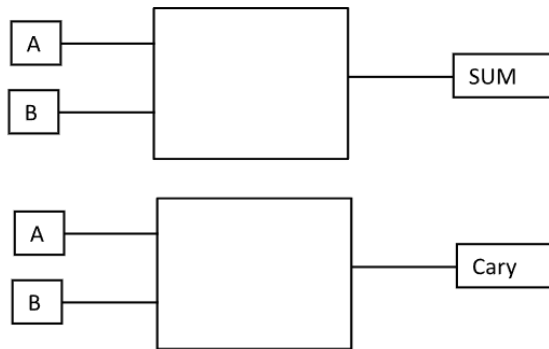4. Represent the sum and the carry-out put using two input logic gates in the following block diagram.



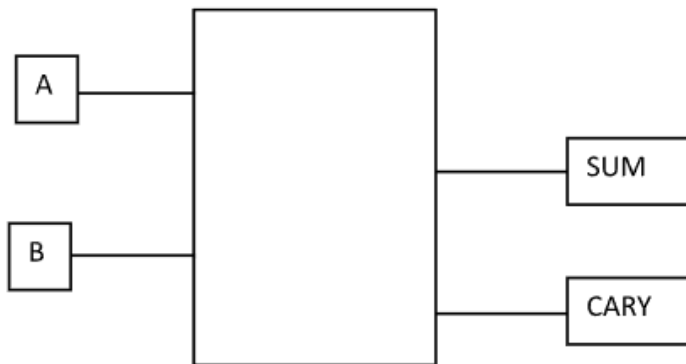5. Using the above logic gates, design a Half Adder logic circuit.



6. Using the above Half Adder circuit design the full adder logic circuit in the following block diagram.

