
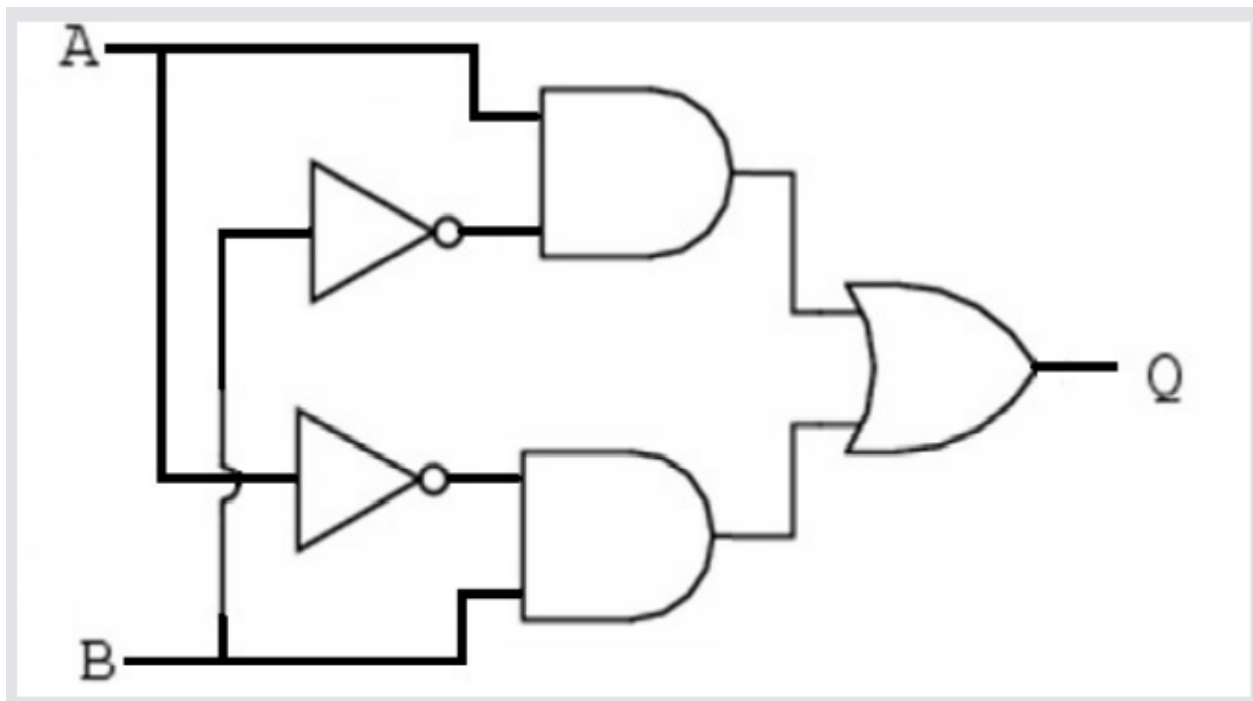



# Tutorial 2

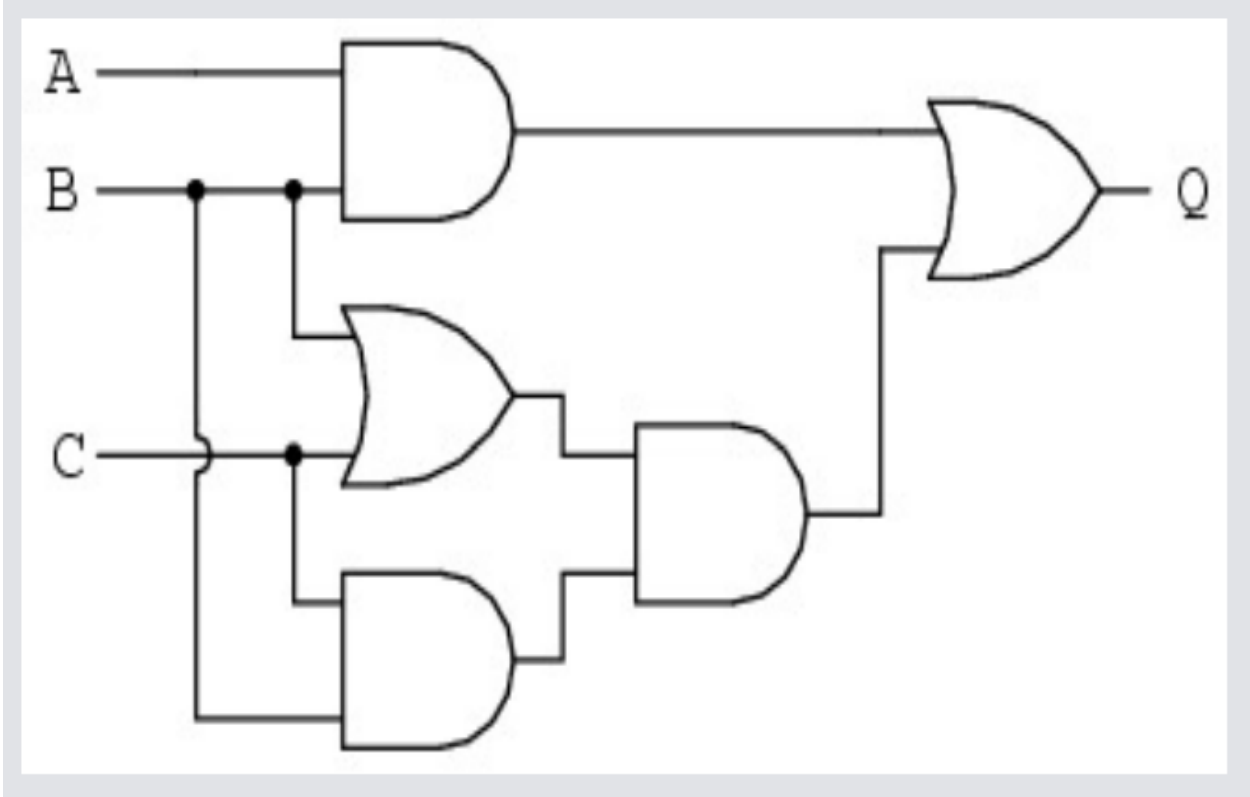1. Find out 3 real world applications of logic gates
2. Derive the boolean expression for the following combinational logic gates





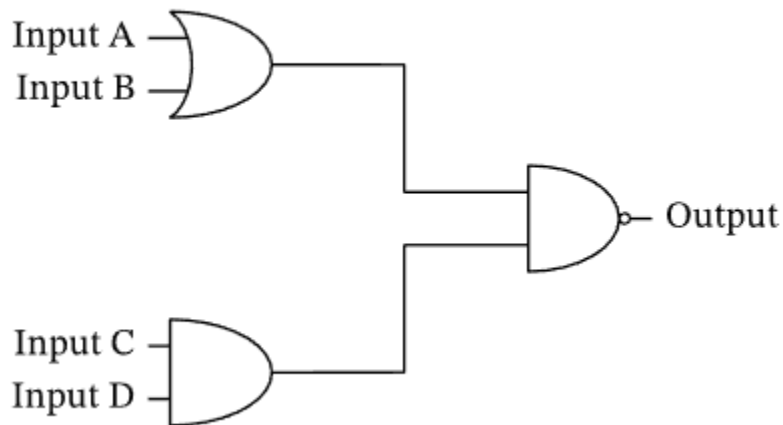
3. The diagram shows a logic circuit consisting of multiple logic gates. The table shows the output for some of the different possible combinations of inputs.



Input A	Input B	Input C	Input D	Output
0	0	0	0	$p$
0	0	1	1	$q$
0	1	0	0	1
0	1	1	1	$r$
1	0	0	0	1
1	0	1	1	$s$
1	1	0	0	1
1	1	1	1	0

1. What is the value of  $p$  in the table?
2. What is the value of  $q$  in the table?
3. What is the value of  $r$  in the table?
4. What is the value of  $s$  in the table?

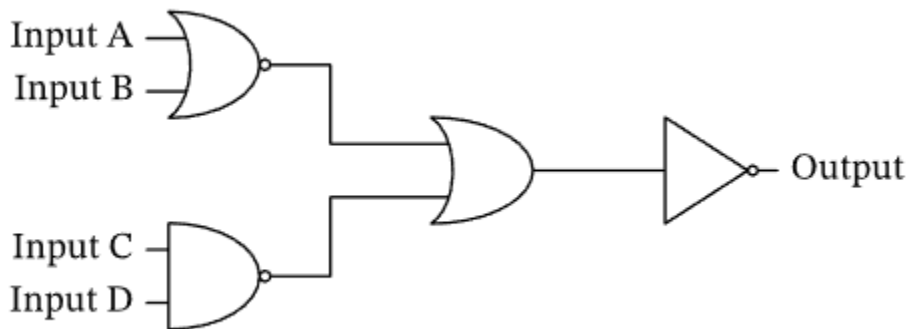4. The diagram shows a logic circuit consisting of multiple logic gates. The table shows the output for some of the different possible combinations of inputs.



Input A	Input B	Input C	Input D	Output
0	0	0	0	$p$
0	1	1	0	$q$
1	0	1	1	$r$
1	1	0	1	$s$

What is the value of  $p$  in the table?

What is the value of  $q$  in the table?

What is the value of  $r$  in the table?

What is the value of  $s$  in the table?